

Programming Assignment 1


A manually created netlist parser

Introduction

- Netlist (net-list)
 - A format of a circuit in the gate-level representation
- Objective
 - Write a program to
 - **read** a circuit described by a pre-defined netlist
 - **simulate** the circuit for two input patterns
 - all primary inputs are 0 and 1, respectively
 - **output** simulation results

Combinational circuits

 - A combinational circuit is composed of **primary inputs**, **primary outputs**, and **logic gates**



- Primary inputs: a , b , c , and d
- Primary outputs: x and y
- Logic gates: $n6$, $n7$, $n8$, and $n9$

Netlist format

- The are **four** parts
 - Comments
 - Primary inputs
 - Primary outputs
 - Logic gates

```
# 4 inputs -- input_data(4)
# 2 outputs -- output_signal(2)
# 6 gates ( 2 BUFFs + 1 NOT + 3 ANDs )
```

```
INPUT(300)
INPUT(301)
INPUT(302)
INPUT(303)
```

```
OUTPUT(400)
OUTPUT(401)
```

```
400 = BUFF(502)
401 = BUFF(503)
```

```
501 = NOT(500)
```

```
500 = AND(300, 301)
502 = AND(501, 302)
503 = AND(302, 303)
```

Comments

- In the beginning of the file, a “#” begins a comment that extends to the **end** of the current line
- Comments give a brief description of the circuit

```
# 4 inputs -- input_data(4)  
# 2 outputs -- output_signal(2)  
# 6 gates ( 2 BUFFs + 1 NOT + 3 ANDs )
```

```
...
```

Primary inputs

- “**INPUT(\$signal_id)**” indicates a primary input, where “**\$signal_id**” is the signal identifier of the primary input
- Every signal identifier is an integer
- Each primary input is listed in one line

...

INPUT(300)

INPUT(301)

INPUT(302)

INPUT(303)

...

Primary outputs

- “**OUTPUT(\$signal_id)**” indicates a primary output, where “**\$signal_id**” is the signal identifier of the primary output
- Every signal identifier is an integer
- Each primary output is listed in one line

...

OUTPUT(400)

OUTPUT(401)

...

Logic gates

- There are 8 types of logic gates as follows
 - #signal_id1 = **BUFF**(\$signal_id2)
 - #signal_id1 = **NOT**(\$signal_id2)
 - #signal_id1 = **AND**(\$signal_id2, \$signal_id3)
 - #signal_id1 = **NAND**(\$signal_id2, \$signal_id3)
 - #signal_id1 = **OR**(\$signal_id2, \$signal_id3)
 - #signal_id1 = **NOR**(\$signal_id2, \$signal_id3)
 - #signal_id1 = **XOR**(\$signal_id2, \$signal_id3)
 - #signal_id1 = **NXOR**(\$signal_id2, \$signal_id3)
- **#signal_id1**: output signal
- **#signal_id2** and **#signal_id3**: input signals
- Every signal identifier is an integer
- Each gate is described in one line

Example

4 inputs -- input_data(4)
2 outputs -- output_signal(2)
6 gates (2 BUFFs + 1 NOT + 3 ANDs)


INPUT(300)
INPUT(301)
INPUT(302)
INPUT(303)

OUTPUT(400)
OUTPUT(401)

400 = BUFF(502)
401 = BUFF(503)

501 = NOT(500)

 500 = AND(300, 301)
502 = AND(501, 302)
503 = AND(302, 303)



Requirement

- In addition to the objective, your program should be executable on the Moon workstation (moon.cse.yzu.edu.tw) with the following method:

```
>> ./a.out < design_00.isc
```


Where a.out is the execution file and design_00.isc is the input file

Output of your program

- Output values of the two input patterns
 - All primary inputs are **0** and **1**, respectively
- For example

00

01

 

Two issues you need to address

- How to store a combinational circuit
 - Directed acyclic graph
- How to simulate a combinational circuit
 - For a gate, before computing the output value, you need to compute all the input values
 - Thus, you need to find the **topological sort order** of the circuit, before you simulate the circuit

Delivery

- Your source code
- A readme describing how to compile and execute your code
- The execution results obtained by **PrintScr** for processing all the given benchmarks
- Upload all the files to Portal by **10/3(Tue.)**
 - No late delivery is allowed